

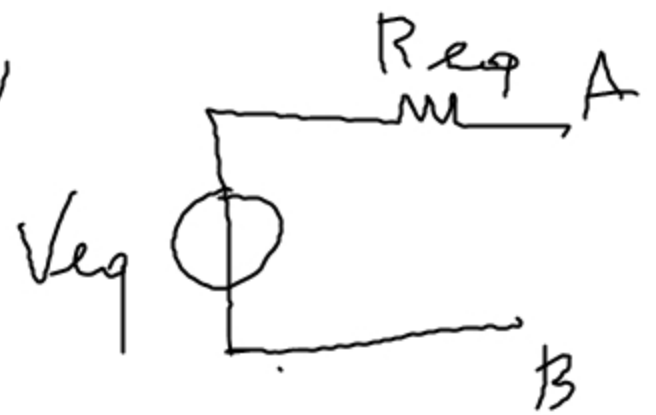


THEVENIN

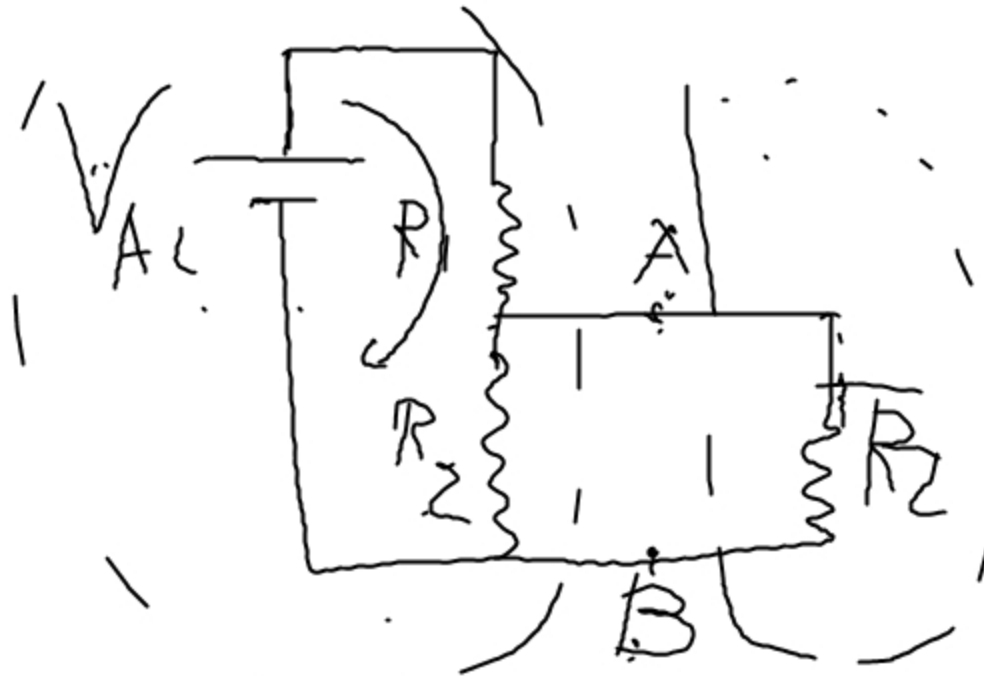


NORTON

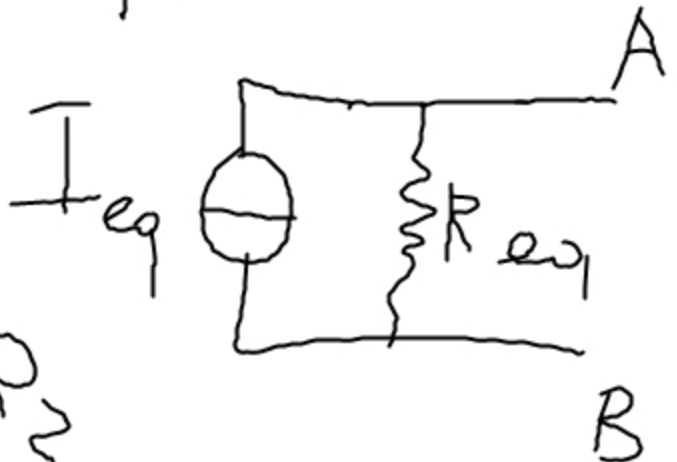


$$V_{AB} = V_{eq} = \frac{V_{AL} \cdot R_2}{R_1 + R_2}$$
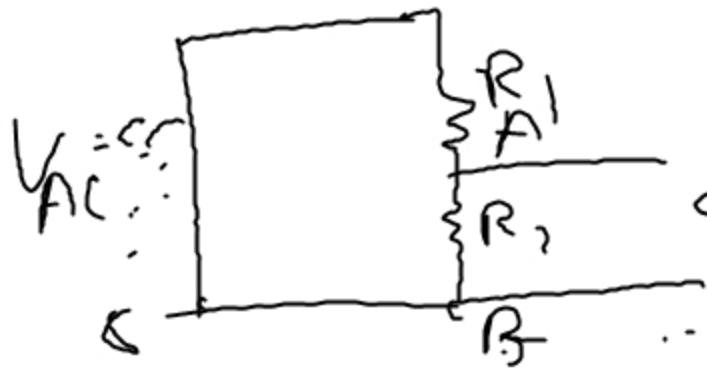
$$I = \frac{V_{AL}}{R_1 + R_2} \Rightarrow V_{AB} = I \cdot R_2 = \frac{V_{AL} \cdot R_2}{R_1 + R_2}$$



$$R_{eq} = R_1 // R_2$$

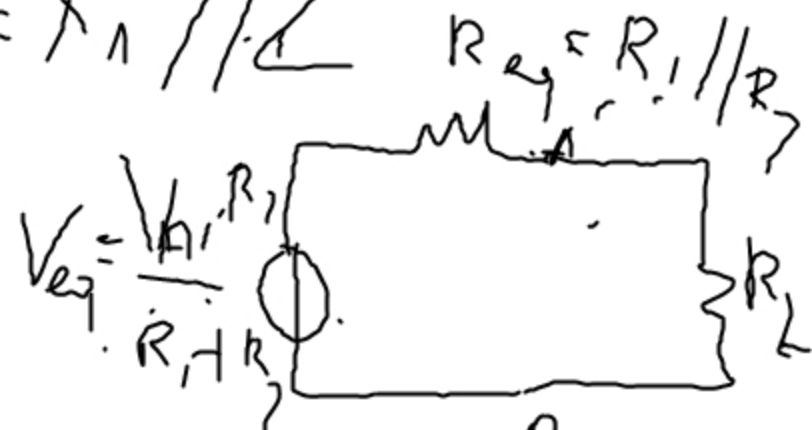


$$I_{eq} = \frac{V_{A2}}{A R_2}$$

$$I_L = \frac{V_{eq}}{R_{eq} + R_L}$$
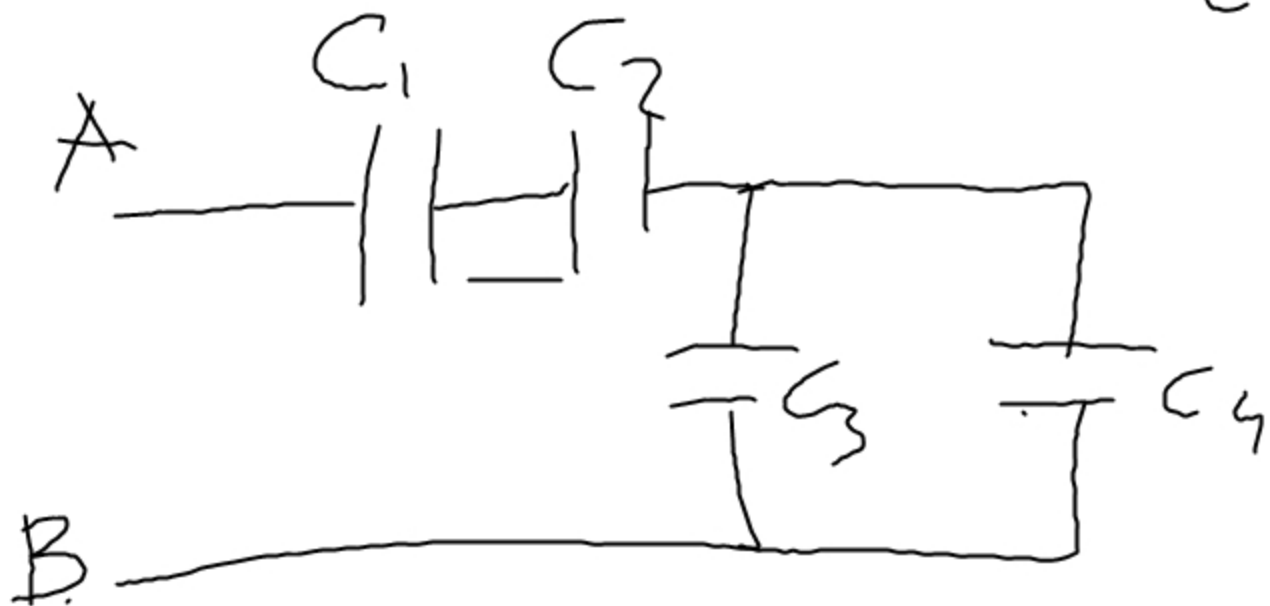
$$V_{A \cdot B} = R_L \cdot I_L = I_{eq} \cdot R_{eq} \cdot \frac{V_{A2}}{R_2}$$





$$C_1 = C_2 = C_3 = C_4 = 1 \mu F$$


$$C_{12} = \frac{C_1 \cdot C_2}{C_1 + C_2} = \frac{1 \cdot 1}{1 + 1} = 0,5 \mu F$$

$$C_{34} = C_3 + C_4 = 1 + 1 = 2 \mu F$$


$$C_{TOT} = \frac{C_{12} \cdot C_{34}}{C_{12} + C_{34}} = \frac{0,5 \cdot 2}{0,5 + 2} = 1 \mu F$$

$$C_{12} = \frac{C_1 \cdot C_2}{C_1 + C_2} = \frac{1}{2} \mu F$$

$$C_{34} = C_3 + C_4 = 2 \mu F$$

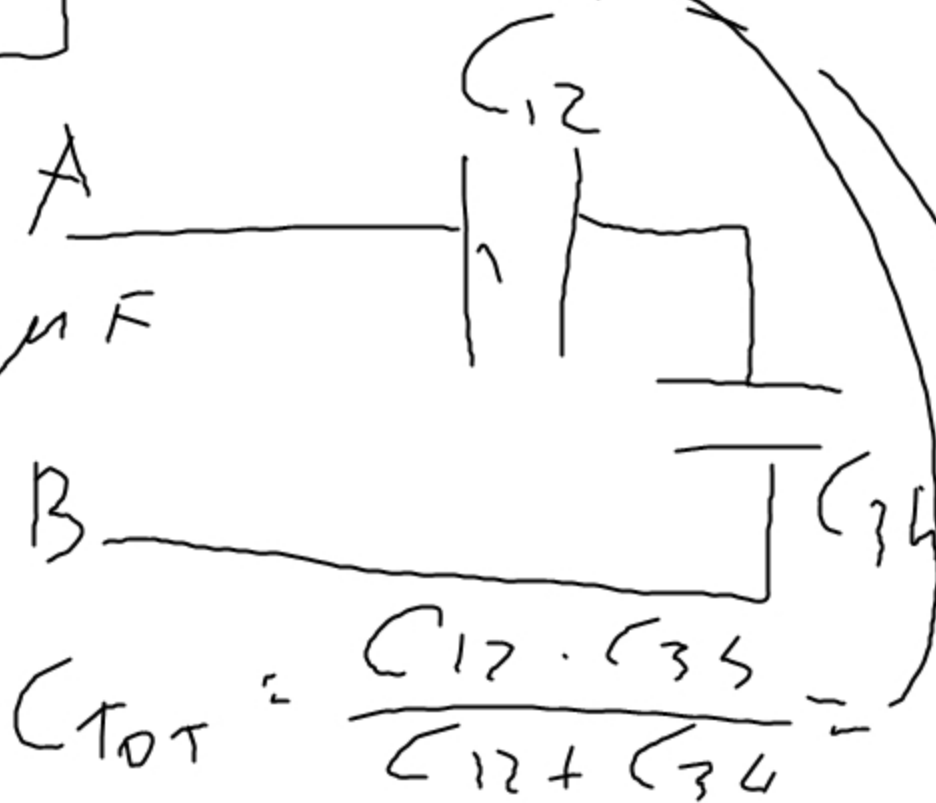
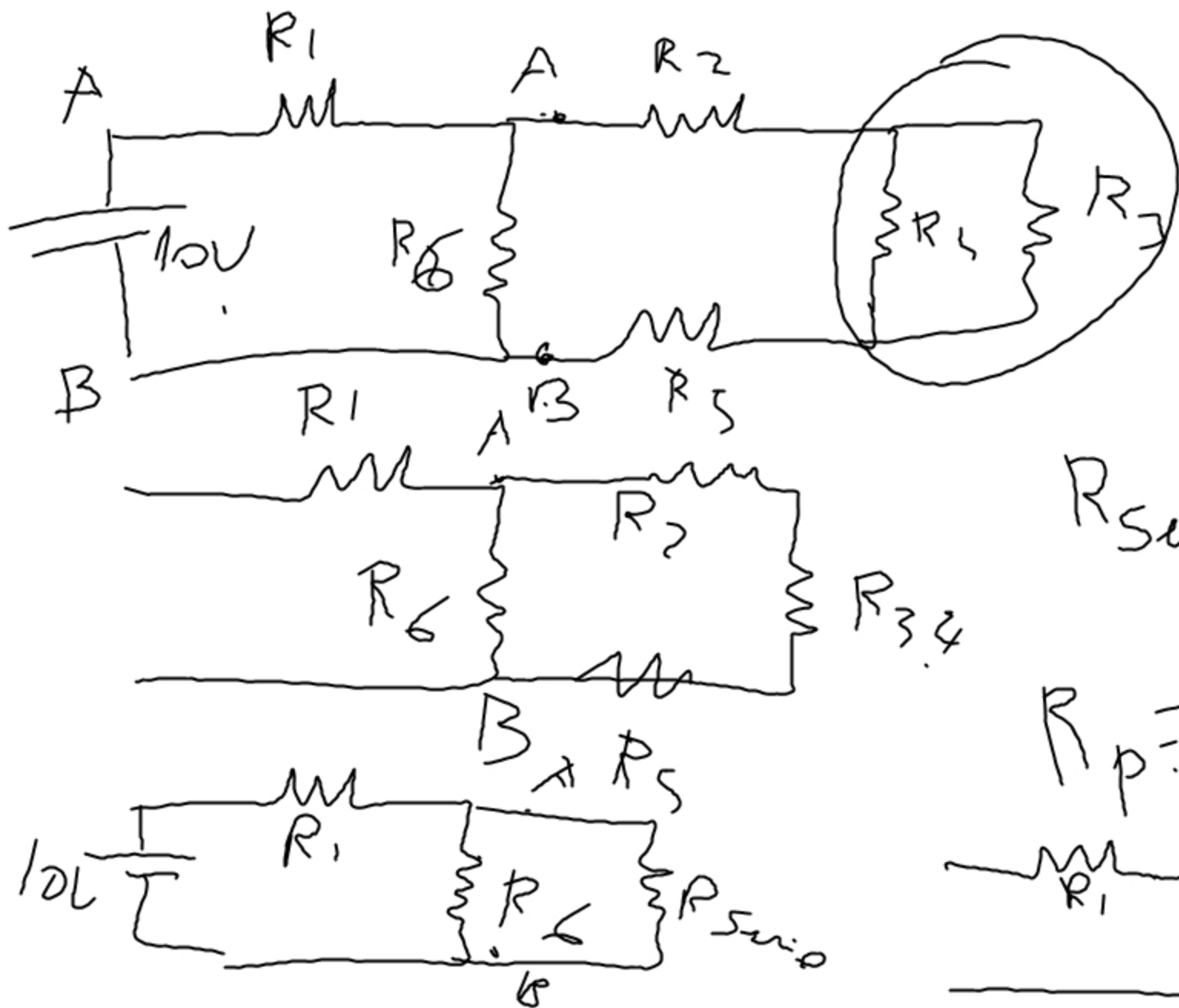
$$C_{TOT} = \frac{C_{12} \cdot C_{34}}{C_{12} + C_{34}} = 1 \mu F$$




$$R_{3,4} = \frac{R_3 \cdot R_4}{R_3 + R_4}$$

$$R_{\text{series}} = R_2 + R_{3,4}$$

$$R_p = R_6 \parallel R_{\text{series}}$$


$$R_T = R_1 + R_p$$
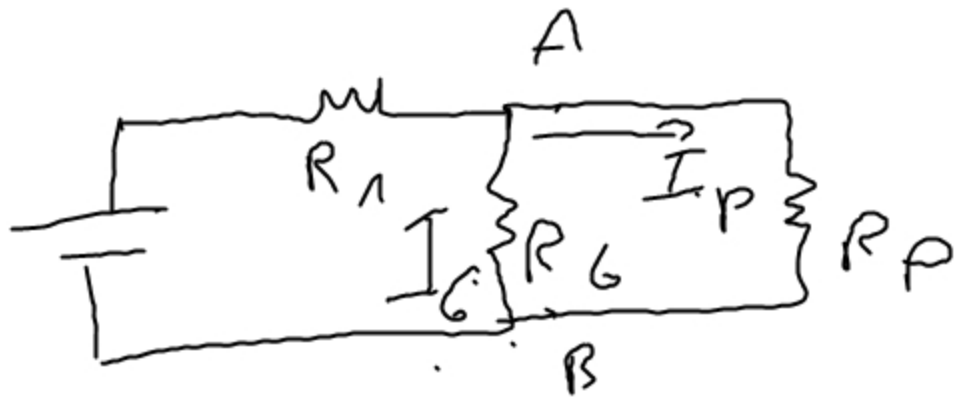
$$V_{AB} = \frac{V_{AL} \cdot R_6}{R_1 + R_6}$$




$$I_6 = \frac{V_{AB}}{R_6}$$

$$I_p = \frac{V_{AB}}{R_p}$$

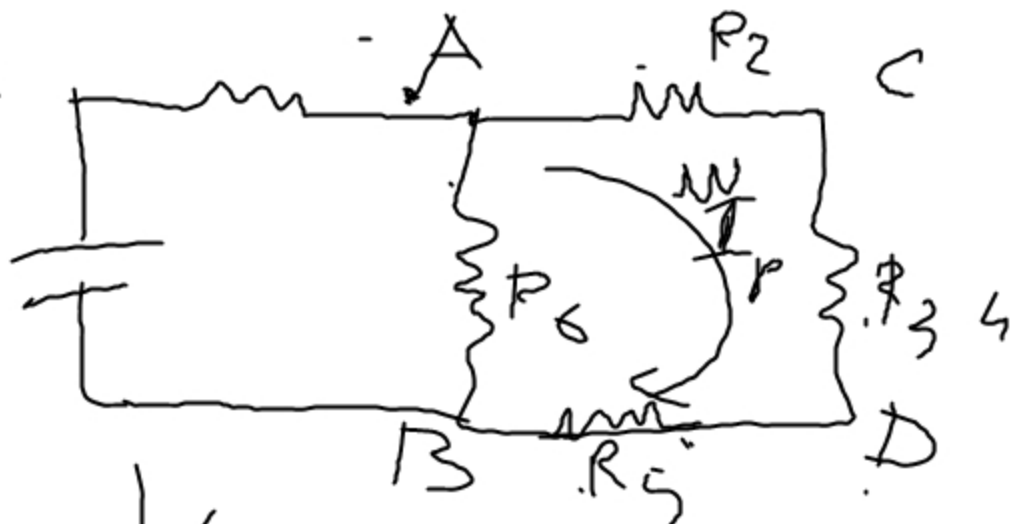

$$V_{R2} = R_2 \cdot I_p$$

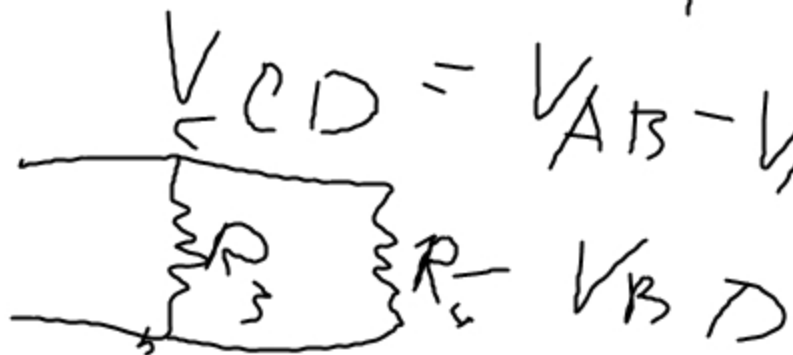

$$V_{CD} = V_{AB} - V_{AC} - V_{R5} = R_5 \cdot I_p$$

