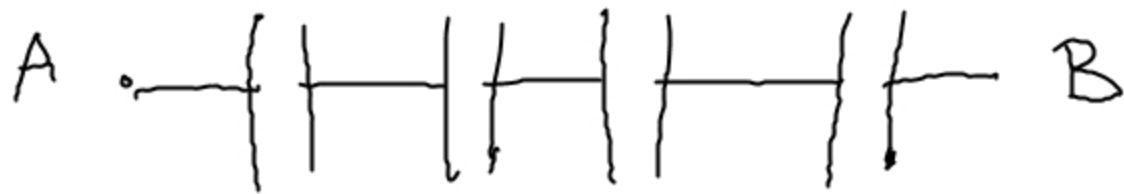


CONDENSATORS IN SERIE



CONDENSATORS IN SERIE

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$$

$$C = \frac{Q}{V}$$


$$C = \frac{\Delta Q}{\Delta V}$$

$$I = \frac{\Delta Q}{\Delta t} = C \cdot \frac{\Delta V}{\Delta t}$$

$$V = R \cdot I$$

$$\frac{\Delta V}{\Delta t} = \frac{R}{C} \cdot I$$

DUE CONDENSATORI IN SERIE

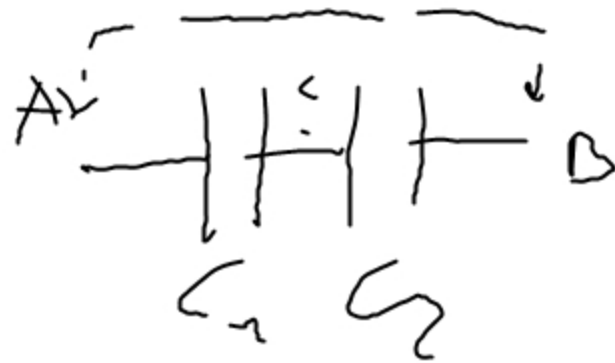


$$V_{AB} = V_{A1} + V_{C2}$$

$$\frac{1}{C_{TOT}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow$$

$$\Rightarrow C_{TOT} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

C_{TOT} = CAPACITÀ TOTALE

CONDENSATORI IN PARALLELO

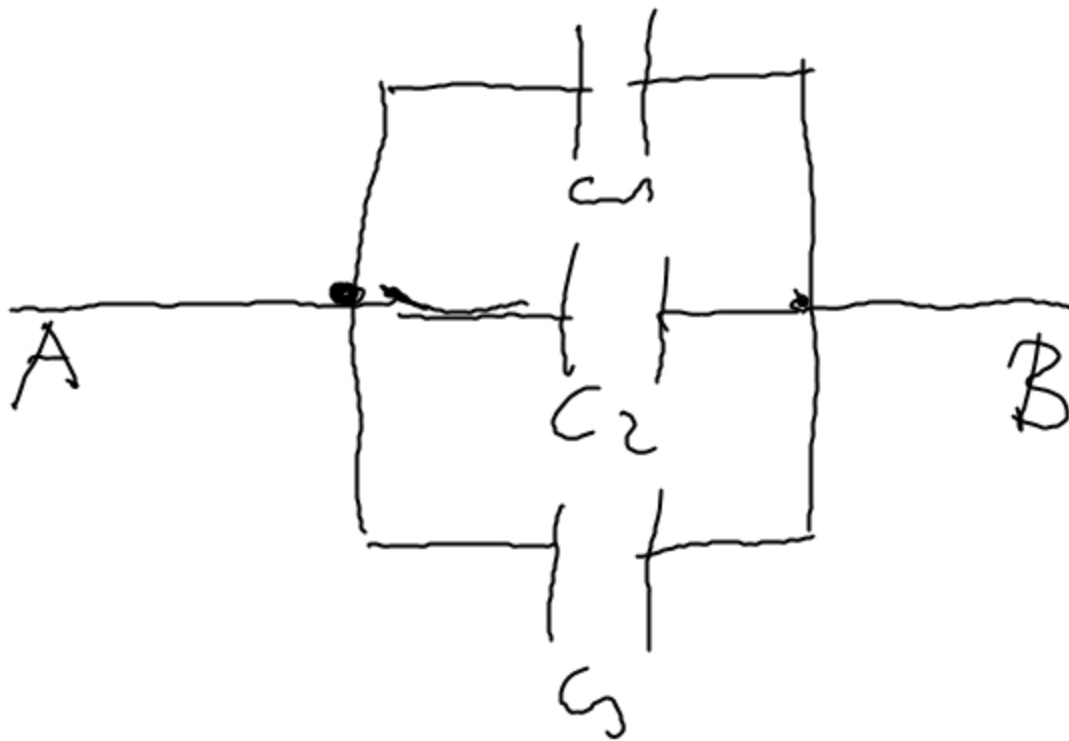

$$C_{TOT} = C_{eq} = C_1 + C_2 + C_3$$

$$V_{AB} = V_{C_1} = V_{C_2} = V_{C_3}$$

es: Three capacitors in parallel

$$C_1 = C_2 = C_3 = 10 \mu\text{F}$$

Wohlfür C_{TOT}


$$C_{TOT} = 10 \mu\text{F} + 10 \mu\text{F} + 10 \mu\text{F} = 30 \mu\text{F}$$

es: Three capacitors in series

$$C_1 = C_2 = C_3 = 10 \mu\text{F}$$

$$C_{TOT} = \frac{1}{\frac{1}{10 \cdot 10^{-6}} + \frac{1}{10 \cdot 10^{-6}} + \frac{1}{10 \cdot 10^{-6}}} = \frac{1}{\frac{3}{10 \cdot 10^{-6}}} = \frac{10 \cdot 10^{-6}}{3} = 3,3 \mu\text{F}$$

L'INDUTTORE

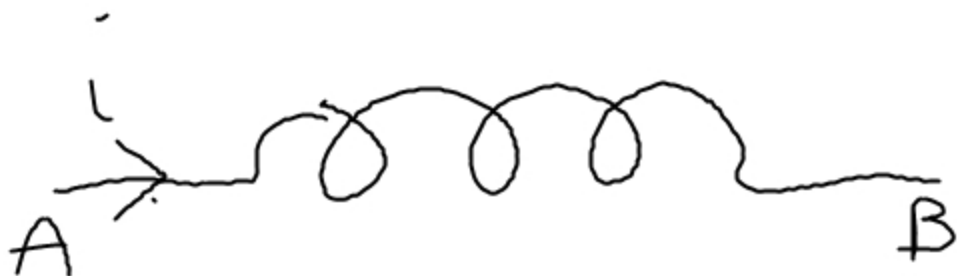

INDUTTANZA

$$L = \frac{\Psi}{I} = [\text{HENRY}]$$



$$V = \frac{\Delta \Psi}{\Delta t} = L \cdot \frac{\Delta I}{\Delta t}$$

La bobina su cui circola corrente

Ψ flusso del campo magnetico concatenato con la bobina

INDUTTANZE IN SERIE



$$L_{TOT} = L_1 + L_2 + L_3$$

INDUTTANZE IN PARALLELO



$$\frac{1}{L_{TOT}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

